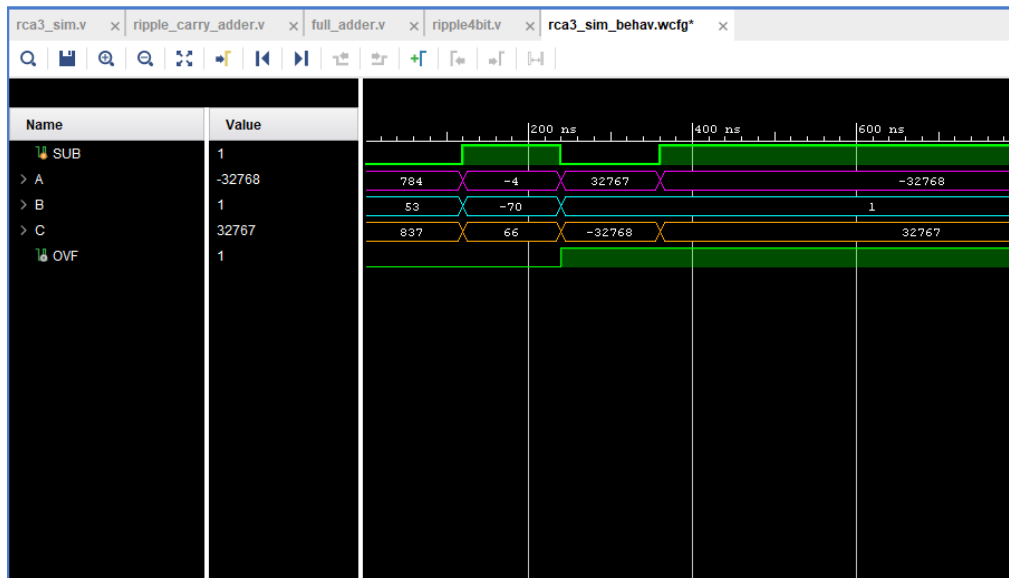



For 16-bit ripple-carry adder-subtractor:

1. Input A = 784, Input B = 53, Operation: Addition → Output C = 837, Overflow = 0
2. Input A = -4, Input B = 70, Operation: Subtraction → Output C = 66, Overflow = 0
3. Input A = 32767, Input B = 1, Operation: Addition → Output C = -32768, Overflow = 1
4. Input A = -32768, Input B = 1, Operation: Subtraction → Output C = 32767, Overflow = 1



For 16-bit hybrid adder-subtractor using four 4-bit carry lookahead adders:

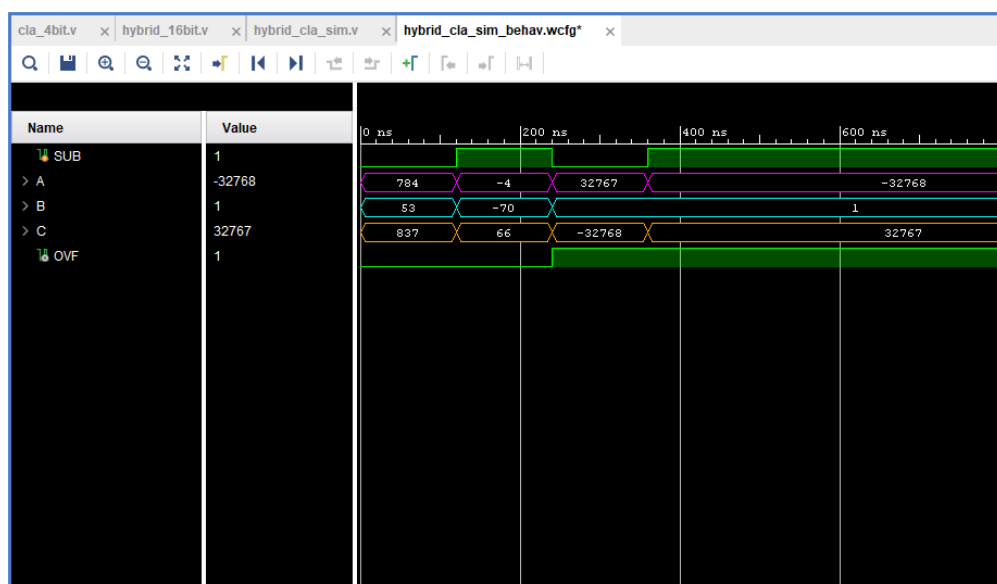5. Input A = 784, Input B = 53, Operation: Addition → Output C = 837, Overflow = 0
6. Input A = -4, Input B = -70, Operation: Subtraction → Output C = 66, Overflow = 0
7. Input A = 32767, Input B = 1, Operation: Addition → Output C = -32768, Overflow = 1
8. Input A = -32768, Input B = 1, Operation: Subtraction → Output C = 32767, Overflow = 1



- Ripple-carry adder is better in terms of area, but the hybrid implementation using four 4-bit carry-lookahead adders is faster since there is no need to wait for computing carry_j in order to compute carry_i, where $i > j$.

- Below, you can see post-implementation project summaries for **16-bit hybrid adder-subtractor using four 4-bit CLA**:

| Utilization | | | |
|---------------|-------------|----------------|---------------------|
| | | Post-Synthesis | Post-Implementation |
| Graph Table | | | |
| Resource | Utilization | Available | Utilization... |
| LUT | 30 | 63400 | 0.05 |
| IO | 50 | 210 | 23.81 |

- Below, you can see post-implementation project summaries for **16-bit ripple-carry adder using full-adders**:

| Graph Table | | | |
|---------------|-------------|-----------|----------------|
| Resource | Utilization | Available | Utilization... |
| LUT | 23 | 63400 | 0.04 |
| IO | 50 | 210 | 23.81 |

- These project summaries indeed verify the fact that ripple-carry adder requires less area.